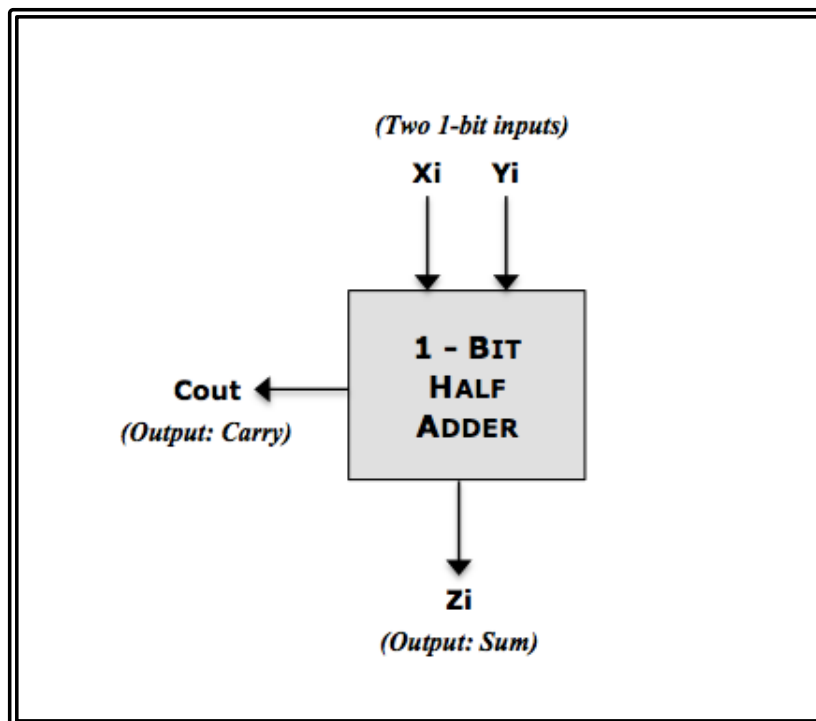


INTEGER DATA COMPUTATION

ONE BIT ADDITION: HALF ADDER

- 1) It is a simple 1-bit adder circuit.
- 2) It adds two 1-bit inputs X_i & Y_i and produces a sum Z_i and a Carry C_{out} .
- 3) As it does not consider any carry input, it can't be combined to add large numbers.
- 4) Hence it is called a Half Adder.



Inputs bits: X_i and Y_i .

Output (Sum): Z_i

Output (Carry): C_{out}

Formula:


Sum (Z_i) = X_i Ex-Or Y_i .

Carry (C_{out}) = $X_i \cdot Y_i$



ONE BIT ADDITION: FULL ADDER

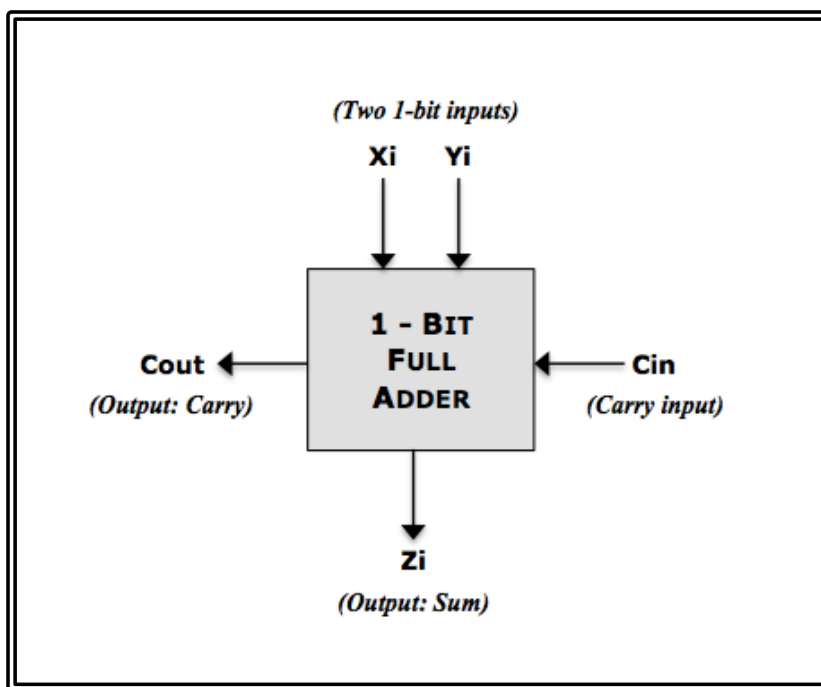- 1) It is a **1-bit adder** circuit.
- 2) It adds **two 1-bit inputs X_i & Y_i** , along with a **Carry Input C_{in}** .
- 3) It produces a **sum Z_i** and a Carry output **C_{out}** .
- 4) As it considers a carry input, it can be used in **combination to add large numbers**.
- 5) Hence it is called a **Full Adder**.



Inputs bits: X_i and Y_i .

Input Carry: C_{in}

Output (Sum): Z_i

Output (Carry): C_{out}

Formula for Sum (Z_i)



$$Z_i = X_i \oplus Y_i \oplus C_{in}$$

$$\therefore Z_i = X_i \cdot Y_i \cdot C_{in} + X_i \cdot Y_i \cdot \overline{C_{in}} + X_i \cdot \overline{Y_i} \cdot C_{in} + \overline{X_i} \cdot Y_i \cdot C_{in}$$

Formula for Carry (C_{out})

$$C_{out} = X_i \cdot Y_i + X_i \cdot C_{in} + Y_i \cdot C_{in}$$

CIRCUIT FOR A FULL ADDER

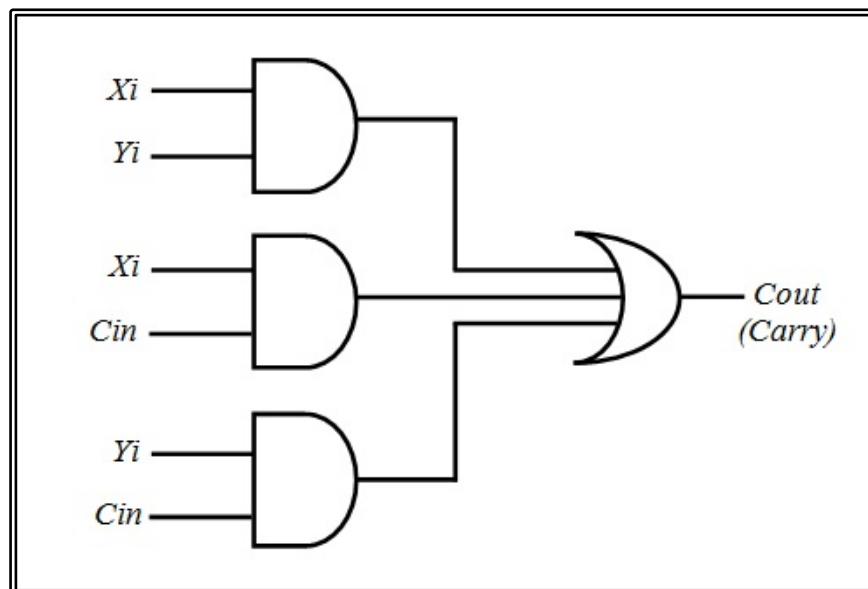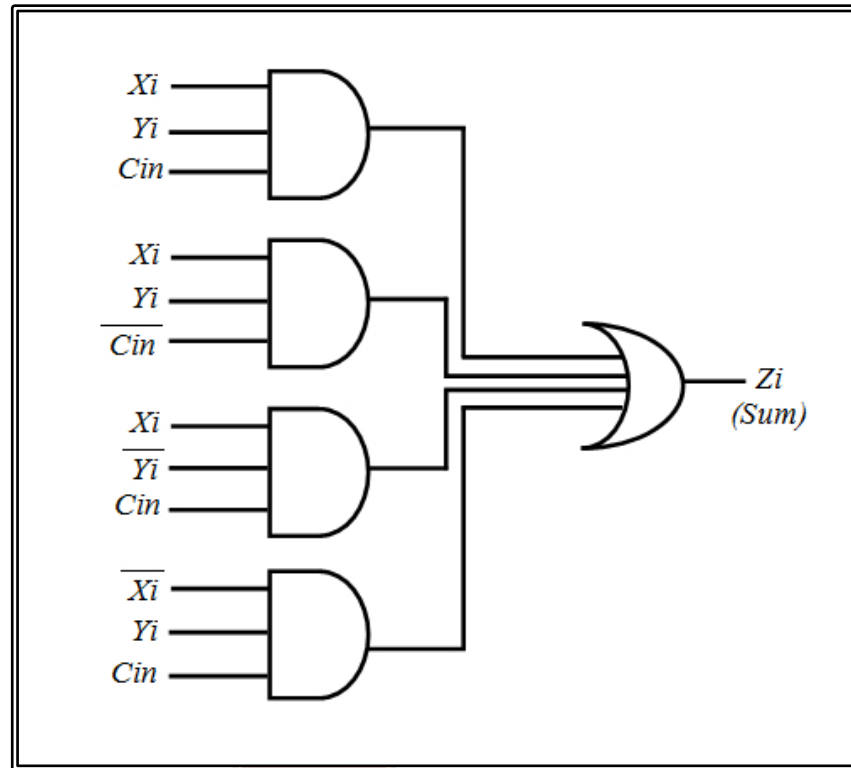



MULTIPLE BIT ADDITION: SERIAL ADDER / RIPPLE CARRY ADDER

- 1) A Full Adder can add two "1-bit" numbers with a Carry input.
- 2) It produces a "1-bit" Sum and a Carry output.
- 3) **Combining many of these Full Adders, we can add multiple bits.**
- 4) One such method is called Serial Adder.
- 5) Here, bits are **added one-by-one from LSB onwards.**
- 6) The **Carry of each stage is propagated (Rippled) into the next stage.**
- 7) Hence, these adders are also called **Ripple Carry Adders.**
- 8) Advantage: They are very **easy to construct.**
- 9) Drawback: As addition happens **bit-by-bit**, they are **slow.**
- 10) **Number of cycles** needed for the addition is equal to the **number of bits to be added.**

Inputs:

Assume X and Y are two "4-bit" numbers to be added, along with a Carry input C_{IN} .

$X = X_0 X_1 X_2 X_3$ (X_0 is the MSB ... X_3 is the LSB)

$Y = Y_0 Y_1 Y_2 Y_3$ (Y_0 is the MSB ... Y_3 is the LSB)

C_{IN} = Carry Input


Outputs:

Assume Z to be a "4-bit" output, and C_{OUT} to be the output Carry

$Z = Z_0 Z_1 Z_2 Z_3$ (Z_0 is the MSB ... Z_3 is the LSB)

C_{OUT} = Carry Output

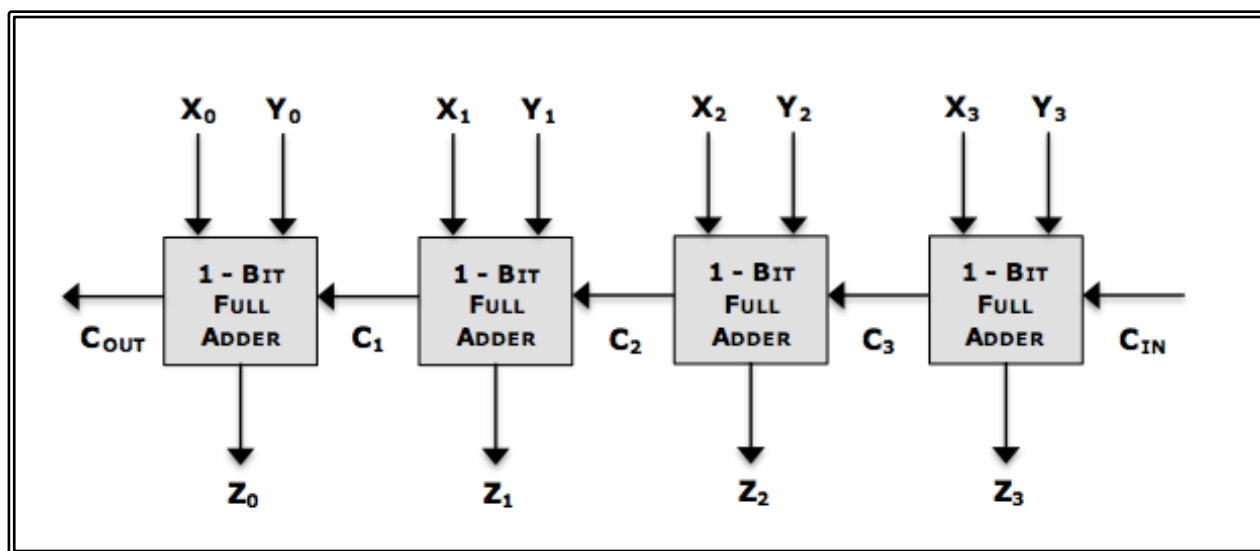Circuit for 4-bit Serial Adder/ Ripple Carry Adder



MULTIPLE BIT ADDITION: CARRY LOOK AHEAD ADDER / PARALLEL ADDER

- 1) It is used to add multiple bits **simultaneously**.
- 2) While adding multiple bits, the main issue is that of the **intermediate carries**.
- 3) In Serial Adders, we therefore added the bits one-by-one.
- 4) This allowed the carry at any stage to propagate to the next stage.
- 5) But this also made the process **very slow**.
- 6) If we "**PREDICT**" the **intermediate carries**, then all bits can be added **simultaneously**.
- 7) This is done by the **Carry Look Ahead Generator** Circuit.
- 8) Once all carries are determined beforehand, then all bits can be **added simultaneously**.
- 9) Advantage: This makes the addition process **extremely fast**.
- 10) Drawback: Circuit is **complex**.

Inputs:

Assume X and Y are two "4-bit" numbers to be added, along with a Carry input C_{IN} .


$X = X_0 X_1 X_2 X_3$ (X_0 is the MSB ... X_3 is the LSB); $Y = Y_0 Y_1 Y_2 Y_3$ & C_{IN} = Carry Input

Outputs:

Assume Z to be a "4-bit" output, and C_{OUT} to be the output Carry

$Z = Z_0 Z_1 Z_2 Z_3$ & C_{OUT} = Carry Output

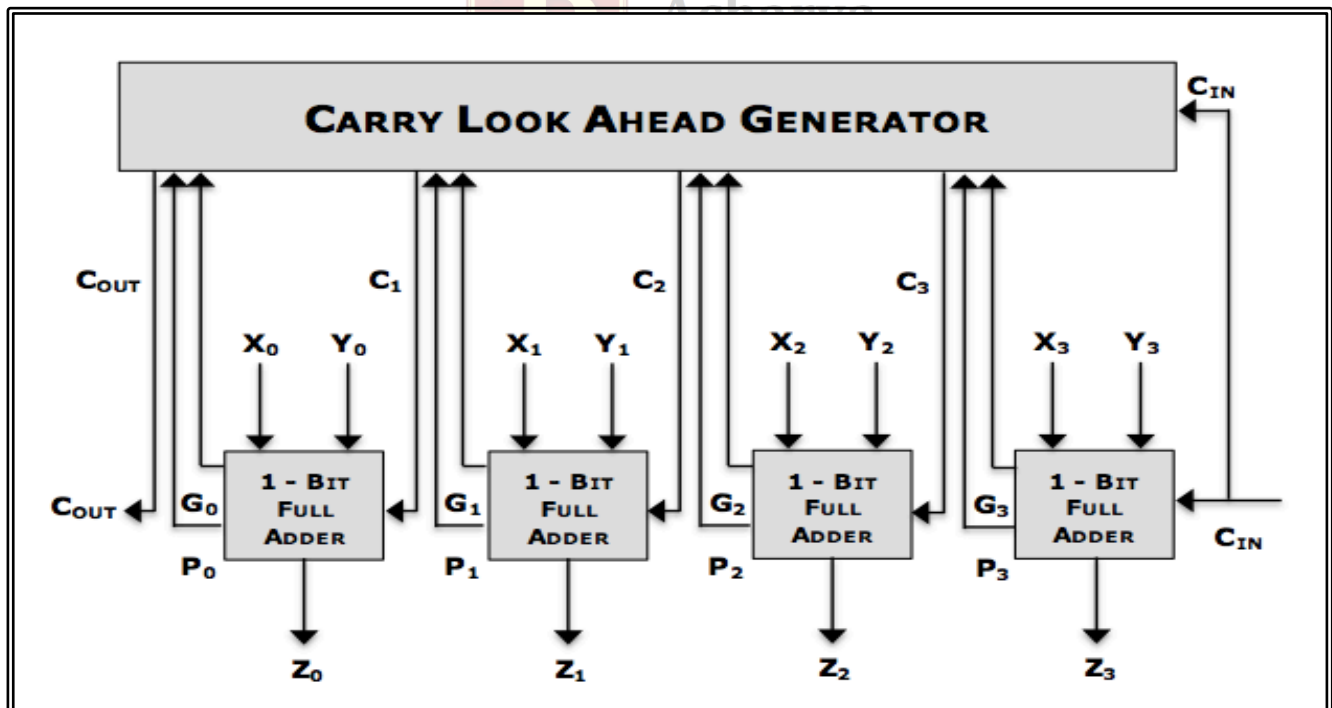Circuit for 4-bit Serial Adder/ Ripple Carry Adder



CALCULATIONS

We can "Predict" (Look Ahead) all the intermediate carries in the following manner.

The Carry at any stage can be calculated as:

$$C_i = X_i \cdot Y_i + X_i \cdot C_{in} + Y_i \cdot C_{in}$$

$$C_i = X_i \cdot Y_i + C_{in}(X_i + Y_i)$$

$$C_i = G_i + P_i \cdot C_{IN}$$

Here $G_i = X_i \cdot Y_i$... (Generate)

And $P_i = X_i + Y_i$... (Propagate)

We need to predict the Carries: C_3 , C_2 , C_1 and C_0

$$C_3 = G_3 + P_3 C_{IN}$$

... I

$$C_2 = G_2 + P_2 C_3$$

Substituting the value of C_3 , we get:

$$C_2 = G_2 + P_2 G_3 + P_2 P_3 C_{IN}$$

... II

$$C_1 = G_1 + P_1 C_2$$

Substituting the value of C_2 , we get:

$$C_1 = G_1 + P_1 G_2 + P_1 P_2 G_3 + P_1 P_2 P_3 C_{IN}$$

... III

$$C_0 = G_0 + P_0 C_1$$

Substituting the value of C_1 , we get:

$$C_0 = G_0 + P_0 G_1 + P_0 P_1 G_2 + P_0 P_1 P_2 G_3 + P_0 P_1 P_2 P_3 C_{IN}$$

... IV

From the above four equations, it is clear that the values of all the four Carries (C_3 , C_2 , C_1 , C_0) can be determined beforehand even without doing the respective additions. To do this we need the values of all G 's ($X_i \cdot Y_i$) and all P 's ($X_i + Y_i$) and the original carry input C_{IN} . This is done by the Carry Look Ahead Generator Circuit.

ADDER / SUBTRACTOR CIRCUIT:

- 1) **Subtraction** in binary numbers is simply performed by **addition of two's complement**.
- 2) That means, a special circuit for subtraction is not needed.
- 3) The same circuit that is used for Addition, can also be used for subtraction.
- 4) The following circuit is called **Adder/ Subtractor** circuit.
- 5) It can perform Addition as $Z = X + Y$.
- 6) It can also perform subtraction as $Z = X + (2\text{'s Complement of } Y)$
- 7) The Variable "S" determines if Addition or Subtraction will be performed.
- 8) **If $S = 0$, then Addition will be performed.**
- 9) **If $S = 1$, then Subtraction will be performed.**
- 10) If $S = 1$, then the operation is $Z = X + (1\text{'s Complement of } Y) + 1$. Hence $Z = X - Y$.

